

402058 – Electronic Circuit Design 1 – Fall 2016

Quiz 1

(08/16/2016)

Student Name: _____ Student No. _____

Honor Code Statement: *I have neither given nor received help on this quiz.* Signature: _____

1. Write the expression of i_1 in terms of I_{in} : _____

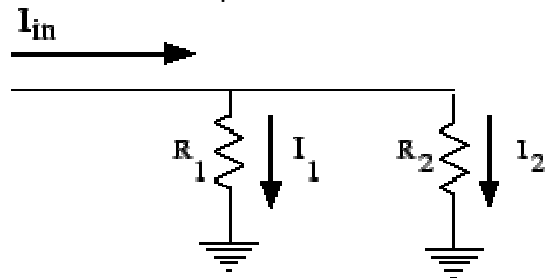


Fig. 1

2. Write the expression of v_{out} in terms of v_{in} : _____

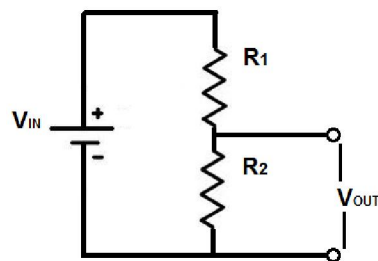


Fig. 2


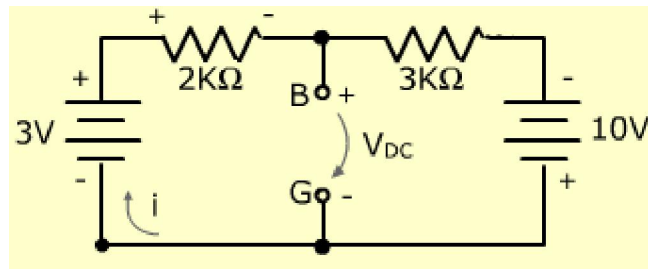


Fig. 3


3. Find the Thevenin equivalent circuit of the circuit in Fig. 3 (seen from B-G):

$V_{TH} =$ _____, $R_{TH} =$ _____

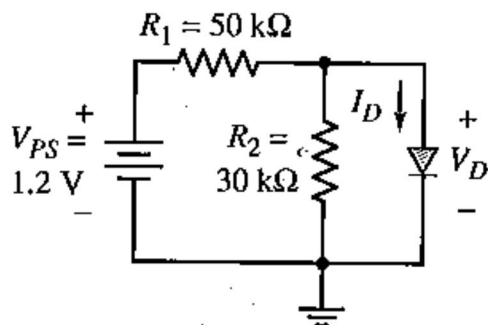
4. What is I_D in the circuit shown below, assume $V_{on}=0.7V$? _____



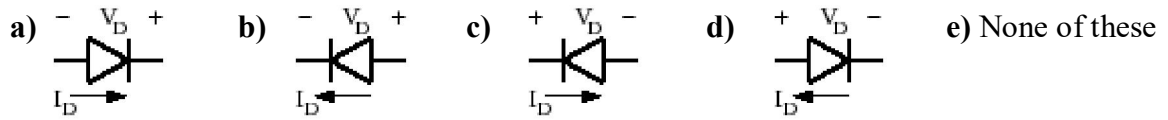5. Which figure above shows the correct sign convention for both positive diode voltage and positive diode current? _____



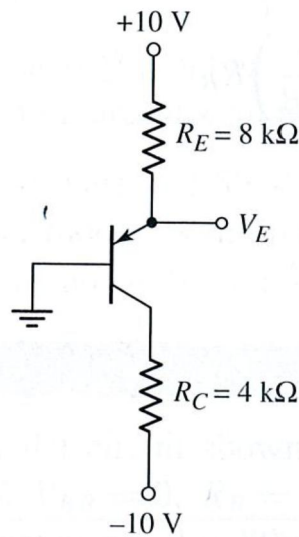6. What is the V_{EC} in the circuit shown below, assume $\beta=85$, $I_s=10^{-14}A$, $V_{EB(ON)}=0.7V$, and $V_T=25mV$?
 $V_{EC} =$ _____



7. For each of the three transistors shown below, identify the region of operation (Cutoff, Forward Active, Reverse Active or Saturation) from the list of possible answers given below.

